

**Note: all the simulations are under  $TT\ 25^\circ C$**

### 1. Cascode amplifier (35%)

Design a common-source amplifier with cascode loading as shown in Fig. 1.

With  $V_{DD}=1.8V$ , design the size of  $M_1\sim M_4$ , the bias voltage  $V_{b1}\sim V_{b3}$ , and  $V_{in,DC}$ , to make  $I_D < 5\mu A$ , voltage gain  $|A_v| \geq 45dB$ , and output swing  $\geq 1.2V$ . You need to make sure that **all MOSFETs operate in saturation region**.

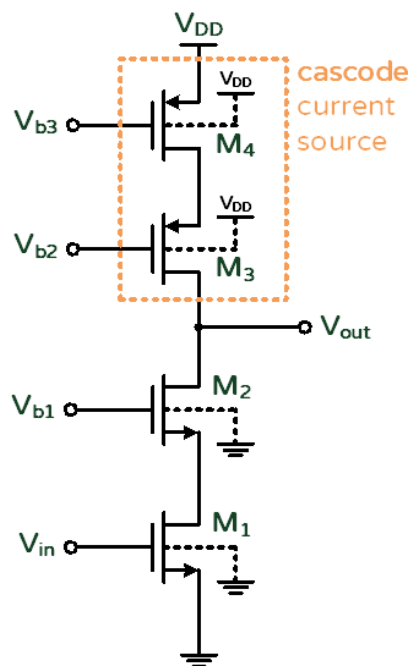


Fig. 1. Cascode structure

- Describe your design consideration. (How you choose the size of  $M_1\sim M_4$ , the bias voltage  $V_{b1}\sim V_{b3}$ , and  $V_{in,DC}$ , to achieve the target performance.) (10%)
- Use “.op” command in Hspice and check the “.lis” file to show that all MOSFETs operate in saturation region, and that  $I_D < 5\mu A$ . (3%)
- Use “.tf” command in Hspice to print out the small signal parameters (gain and output impedance). Confirm that  $|A_v| \geq 45dB$ . (2%)
- Calculate  $A_v$  and output impedance by **hand-calculation**. You can use the parameters in “.lis” from (b). Then compare your answer with the simulation results in (c). (5%)
- Use “.dc” command to sweep  $V_{in}$  from 0V to 1.8V (set **step=0.00001V=10 $\mu$ V**) in Hspice. Show that output swing  $\geq 1.2V$  **under the condition  $|A_v| \geq 45dB$  using WaveView**. (5%)

*Hint: You can use the following Hspice command in your .sp file*

```
.dc Vin_value 0 1.8 10u
.meas DC output_swing_upper_bound Find V(vout) WHEN deriv('V(vout)')=-10^(45/20)' cross=1
.meas DC output_swing_lower_bound Find V(vout) WHEN deriv('V(vout)')=-10^(45/20)' cross=2
.meas DC output_swing_param='output_swing_upper_bound-output_swing_lower_bound'
```

After simulation, you will see the measured value of output\_swing in .ms0 file:

output_swing_upper_bound	output_swing_lower_bound	output_swing
temper	alter#	
1.4574	0.2562	1.2012
1		25.0000

However, this is just for quickly checking output swing for convenience. **You should still show output swing  $\geq 1.2V$  using cursor in WaveView !!**

Hint: You can use the following Hspice command in your .sp file

```
.dc Vin_value 0 1.8 10u
.probe gain=deriv('V(vout)')
```

which is because " $A_v = \frac{\partial V_{out}}{\partial V_{in}}$ ".

After simulation, you can see "gain (V/V) v.s.  $V_{in}$  (V)" waveform in WaveView.

- (f) Calculate **output swing by hand-calculation**. You can use the parameters in ".lis" from (b). Then compare your answer with the simulation result in (e), and **describe** where the error comes from. (5%)
- (g) Please fill in the following specification table. Make sure you achieve all the requirements. (5%)


	specification	simulation	hand-calculation
$V_{DD}$	1.8V		
$M_1$ (W/L, m)	—		
$M_2$ (W/L, m)	—		
$M_3$ (W/L, m)	—		
$M_4$ (W/L, m)	—		
$V_{in,DC}$	—		
$V_{b1}$	—		
$V_{b2}$	—		
$V_{b3}$	—		
$I_D$	$< 5\mu A$		—
gain $ A_v $	$\geq 45dB$		
output impedance	—		
output swing	$\geq 1.2V$		

**Table 1.** Specification table for problem 1.


## 2. Cascade amplifier (55%)

Design a CS-CG cascade amplifier as in Fig. 3.

- (a) As shown in Fig. 2.(a), with  $V_{DD}=1.8V$ , design the common source stage (with ideal current source load, static current= $3\mu A$ ) to make  $V_{out1,DC}=0.5V$  (within  $\pm 10mV$  variation) and voltage gain  $|A_{v1}| \geq 100V/V$ .
- Describe your design consideration (How you choose the size of  $M_1$  and  $V_{in,DC}$ ). (5%)
  - Use “.op” command in Hspice and check the “.lis” file to show that  $M_1$  operates in saturation region, and that  $V_{out1,DC}=0.5V$  (within  $\pm 10mV$  variation) (3%)
  - Use “.tf” command in Hspice to print out the small signal parameters (gain and output impedance). Confirm that  $|A_{v1}| \geq 100V/V$ . (2%)
  - Calculate  $A_{v1}$  **by hand-calculation**. You can use the parameters in “.lis” in (ii.). Then compare your answer with the simulation results in (iii.). (5%)
- (b) As shown in Fig. 2.(b), with  $V_{DD}=1.8V$  and  $V_{in1,DC}=0.5V$ , design the common gate stage to make  $I_D=10\mu A$  (within 1% variation) and voltage gain  $|A_{v2}| \geq 10V/V$ .
- Describe your design consideration (How you choose the size of  $M_2$ , the bias voltage  $V_b$ , and the resistance of  $R_D$ ). (10%)
  - Use “.op” command in Hspice and check the “.lis” file to show that  $M_2$  operates in saturation region, and that  $I_D=10\mu A$  (within 1% variation). (3%)
  - Use “.tf” command in Hspice to print out the small signal parameters (gain, input impedance, and output impedance). Confirm that  $|A_{v2}| \geq 10V/V$ . (2%)
  - Calculate  $A_{v2}$ , input impedance, and output impedance **by hand-calculation**. You can use the parameters in “.lis” in (ii.). Then compare your answer with the simulation results in (iii.). (5%)

 

**Fig. 2.** Two stages in cascade structure. (a) stage 1; (b) stage 2

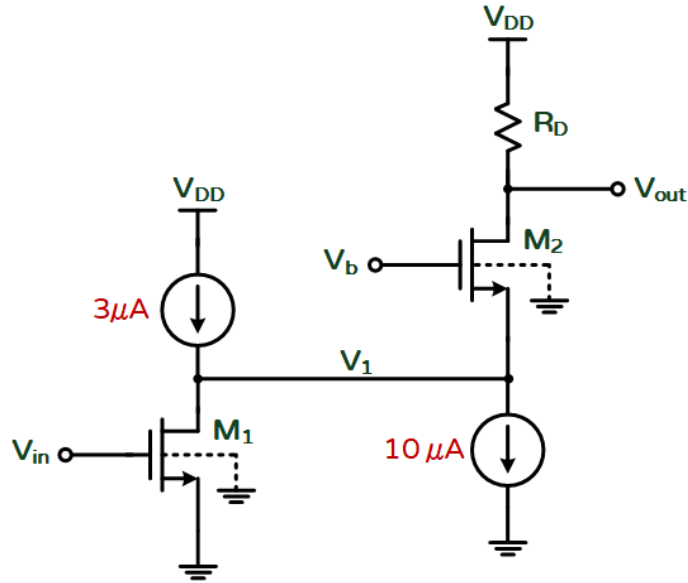

**Fig. 3.** Cascode structure

(c) Connect the above two stages and **add an additional 10μA current source** as shown in Fig. 3.

- Use “.op” command in Hspice and check the “.lis” file: Is the DC bias ( $V_1$ ) still **around 0.5V**? (5%)
- After simulation, whether the overall gain (from  $V_{in}$  to  $V_{out}$ ) equals  $A_{v1} \times A_{v2}$  or not? If not, why not? (5%)
- Please calculate the overall gain by **hand-calculation**, and compare your answer with the simulation results in (ii.). (5%)

(d) Please fill in the following specification table. Make sure you achieve all the requirements. (5%)

	specification	simulation	hand-calculation
<b>Fig. 2.(a) Common-Source stage</b>			
$V_{DD}$	1.8V		
<b>current source load</b>	3μA		
$M_1$ (W/L, m)	—		
$V_{in,DC}$	—		
$V_{out1,DC}$	0.5V±10mV		—
<b>gain</b> $ A_{v1} $	≥ 100V/V		
<b>output impedance</b>	—		—

Fig. 2.(b) Common-Gate stage			
$V_{DD}$	1.8V		
$V_{in1,DC}$	0.5V		
$M_2$ (W/L, m)	–		
$V_b$	–		
$R_D$	–		
$I_D$	$10\mu A \pm 1\%$		–
gain $ A_{v2} $	$\geq 10V/V$		
input impedance	–		
output impedance	–		
Fig. 3. Cascade CS-CG amplifier			
$V_{DD}$	1.8V		
DC bias ( $V_1$ )	–		–
overall gain $ A_v $	–		

**Table 2.** Specification table for problem 2.

### 3. Comparison between “cascode structure” & “cascade structure” (10%)

In this problem, let's discuss the differences between “cascode structure” and “cascade structure”. What are the advantages and drawbacks of each of them? List from **two** points of view, for example, output swing and power. (5% for each)

1.	From _____ point of view, <u>cascode</u> / <u>cascade</u> structure is better than the other one because _____ .
2.	From _____ point of view, <u>cascode</u> / <u>cascade</u> structure is better than the other one because _____ .