

**Note: all the simulations are under TT 25°C**

1. Use Hspice to simulate the DC analysis of Fig.1 with  $V_{dd}=1.8V$  and  $V_{gs}$  from 0V to 1.8V with a step of 0.01V. Please keep the W/L ratio of NMOS and PMOS equal to 3, and sweep channel length of NMOS and PMOS from  $0.5\mu m$  to  $5\mu m$  with a step of  $0.5\mu m$ . Please probe  $I_d$  vs.  $V_{gs}$  with different channel lengths of NMOS and PMOS and discuss your observations.(10%)

(Ref. code: .DC Vgs 0 1.8 0.01 sweep L 0.5u 5u 0.5u)

 


Fig. 1

2. Use Hspice to simulate the diode connected structure as shown at Fig.2 with  $V_{dd}=1.8V$ . Please keep the bias current constant and the W/L ratio of NMOS and PMOS equal to 3, and sweep channel length of NMOS and PMOS from  $0.18\mu m$  to  $10\mu m$  with a step of  $0.01\mu m$ . Please probe the following parameters of NMOS and PMOS and discuss your observations.(40%)

- (a)  $V_{th}$  vs. L
- (b)  $g_{ds}$  vs. L
- (c)  $g_m$  vs. L
- (d)  $g_m/C_g$  vs. L

 


Fig. 2

3. Use Hspice to simulate the capacitance characteristic of NMOS as shown in Fig.3 with body connected to 0V. Please keep  $W/L=1.5\mu\text{m}/0.2\mu\text{m}$  and sweep  $V_G$  from -1.8V to 1.8V. Please probe the following parameters and discuss your observations.(40%)
- (a)  $C_{gs}$  vs.  $V_G$
  - (b)  $C_{gd}$  vs.  $V_G$
  - (c)  $C_{gb}$  vs.  $V_G$
  - (d)  $C_{g\_total}$  vs.  $V_G$

 


Fig. 3

4. **Body effect.** Use Hspice to simulate DC analysis of Fig.4 with  $V_{dd}=1.8\text{V}$  and  $V_b$  from 0V to 1.8V with a step of 0.01V. Please keep the bias current constant and the  $W/L$  ratio of NMOS and PMOS equal to 3, and sweep channel length of NMOS and PMOS from  $0.5\mu\text{m}$  to  $5\mu\text{m}$  with a step of  $0.5\mu\text{m}$ . Please probe  $V_{th}$  vs.  $V_b$  of NMOS and PMOS and discuss your observations.(10%)

 


Fig. 4