

Note: all the simulations are under $TT\ 25^\circ C$

1. Common Source (CS) (50%)

As shown in Fig. 1, we have a common source (CS) stage with $V_{DD}=1.8V$.

Try to design the size of M_1 and the resistance of R_D to achieve AC gain $|A_v| > 3V/V$ and $V_{out,DC} = 0.9V$ (within 1% variation), under the constraint $V_{in,DC} = 0.9V$. You need to make sure that M_1 operates in saturation region.

 


Fig. 1. A common source amplifier

(a) Design this circuit to achieve the requirements:

- (1) M_1 operates in saturation region
- (2) output DC voltage $V_{out,DC} = 0.9V \pm 1\%$
- (3) AC gain $|A_v| > 3$ (V/V)
- (4) the resistance of $R_D < 50k\Omega$

Describe how you choose the size of M_1 and the resistance of R_D to achieve the requirements. (10%)

(b) Use “.op” command in Hspice and check the “.lis” file to show that M_1 operates in saturation region. Screenshot $V_{in,DC}$, $V_{out,DC}$ and drain current (I_D) of M_1 . (5%)

Hint: use the following Hspice command in your .sp file

```
.op
```

After simulation, you will see $V_{in,DC}$ and $V_{out,DC}$ in .lis file:

```
***** operating point status is all simulation time is 0.
node    =voltage node    =voltage node    =voltage
+0:vdd  = 1.8000 0:vin    = Vin,DC 0:vout  = Vout,DC
```

and MOS characteristic parameters (including operation region, I_D , etc.) in .lis file:

```
**** mosfets

subckt
element 0:m1
model   0:n_18.1
region  MOS
id      character-
ibs     istic
ibd     parameters
:
```

- (c) Use “.tf” command in Hspice to print out:
- (1) the small signal gain from V_{in} to V_{out} (2.5%)
 - (2) the output impedance (2.5%)

Hint: use the following Hspice command in your .sp file

```
.tf V(vout) Vin
```

After simulation, you will see small-signal parameters in .lis file:

```
****      small-signal transfer characteristics

v(vout)/vin          = AC gain
input resistance at  vin = Rin
output resistance at v(vout) = Rout
```

- (d) Calculate $V_{out,DC}$, AC gain and output impedance by **hand-calculation**. You can use the parameters in “.lis” file in (b). (10%)

Hint: you won't find “ r_o ” in .lis file. Instead, you can find the value of “ g_{ds} ” and use this relationship “ $r_o = \frac{1}{g_{ds}}$.”

- (e) Compare AC gain and output impedance between those by simulation in (c) and those by hand-calculation in (d). Report the **error rate** ($= \frac{\text{simulation} - \text{hand}}{\text{hand}} \times 100\%$), and **describe** where the error comes from. (10%)

- (f) Please fill in the following specification table. Make sure you achieve all the requirements. (10%)

	Specification	simulation	hand-calculation
V_{DD}	1.8V		
$V_{in,DC}$	0.9V		
M_1 (W/L, m)	—		
R_D	< 50k Ω		
$V_{out,DC}$	0.9V \pm 1%		
gain $ A_v $	> 3V/V		
output impedance	—		
I_D	—		—

Table 1. Specification table for CS

2. Common Gate (CG) (25%)

As shown in Fig. 2, we have a common gate (CG) stage with $V_{DD}=1.8V$.

Try to design the size of M_2 , the bias voltage V_b and the resistance of R_D to achieve AC gain $|A_v| > 9V/V$ and $V_{out,DC} = 0.9V$ (within 1% variation), under the constraint $V_{in,DC} = 0.5V$. You need to make sure that M_2 operates in saturation region.

 


Fig. 2. A common gate amplifier

(a) Design this circuit to achieve the requirements:

- (1) M_2 operates in saturation region
- (2) output DC voltage $V_{out,DC} = 0.9V \pm 1\%$
- (3) AC gain $|A_v| > 9$ (V/V)
- (4) the resistance of $R_D < 100k\Omega$

Describe how you choose the size of M_2 , the bias voltage V_b and the resistance of R_D to achieve the requirements. (5%)

(b) Use “.op” command in Hspice and check the “.lis” file to show that M_2 operates in saturation region. Screenshot $V_{out,DC}$ and drain current (I_D) of M_2 . (2%)

(c) Use “.tf” command in Hspice to print out:

- (1) the small signal gain from V_{in} to V_{out} (1%)
- (2) the input impedance (1%)
- (3) the output impedance (1%)

(d) Calculate $V_{out,DC}$, AC gain, input impedance and output impedance by **hand-calculation**. You can use the parameters in “.lis” file in (b). Compare AC gain, input impedance and output impedance with those by simulation in (c). Report the **error rate** ($= \frac{\text{simulation-hand}}{\text{hand}} \times 100\%$), and **describe** where the error comes from. (10%)

(e) Please fill in the following specification table. Make sure you achieve all the requirements. (5%)

	Specification	simulation	hand-calculation
V_{DD}	1.8V		
$V_{in,DC}$	0.5V		
M_2 (W/L, m)	–		
R_D	$< 100k\Omega$		
$V_{out,DC}$	$0.9V \pm 1\%$		
gain $ A_v $	$> 9V/V$		
input impedance	–		
output impedance	–		
I_D	–		–

Table 2. Specification table for CG

3. Common Drain (CD) (a.k.a. Source Follower, SF) (25%)

As shown in Fig. 3, we have a common drain (CD) stage with $V_{DD}=1.8V$.

Try to design the size of M_3 and the resistance of R_S to achieve AC gain $|A_v| > 0.75V/V$ and $V_{out,DC} = 0.9V$ (within 1% variation), under the constraint $V_{in,DC} = 1.5V$. You need to make sure that M_3 operates in saturation region.

 


Fig. 3. A common drain amplifier

(a) Design this circuit to achieve the requirements:

- (1) M_3 operates in saturation region
- (2) output DC voltage $V_{out,DC} = 0.9V \pm 1\%$
- (3) AC gain $|A_v| > 0.75(V/V)$
- (4) the resistance of $R_S < 80k\Omega$

Describe how you choose the size of M_3 and the resistance of R_S to achieve the requirements. (5%)

(b) Use “.op” command in Hspice and check the “.lis” file to show that M_3 operates in saturation region. Screenshot $V_{out,DC}$ and drain current (I_D) of M_3 . (3%)

(c) Use “.tf” command in Hspice to print out:

- (1) the small signal gain from V_{in} to V_{out} (1%)
- (2) the output impedance (1%)

(d) Calculate $V_{out,DC}$, AC gain and output impedance by hand-calculation. You can use the parameters in “.lis” file in (b). Compare AC gain and output impedance with those by simulation in (c). Report the **error rate** ($= \frac{\text{simulation} - \text{hand}}{\text{hand}} \times 100\%$), and **describe** where the error comes from. (10%)

(e) Please fill in the following specification table. Make sure you achieve all the requirements. (5%)

	Specification	simulation	hand-calculation
V_{DD}	1.8V		
$V_{in,DC}$	1.5V		
M_3 (W/L, m)	—		
R_S	$< 80k\Omega$		
$V_{out,DC}$	$0.9V \pm 1\%$		
gain $ A_v $	$> 0.75V/V$		
output impedance	—		
I_D	—		—

Table 3. Specification table for CD